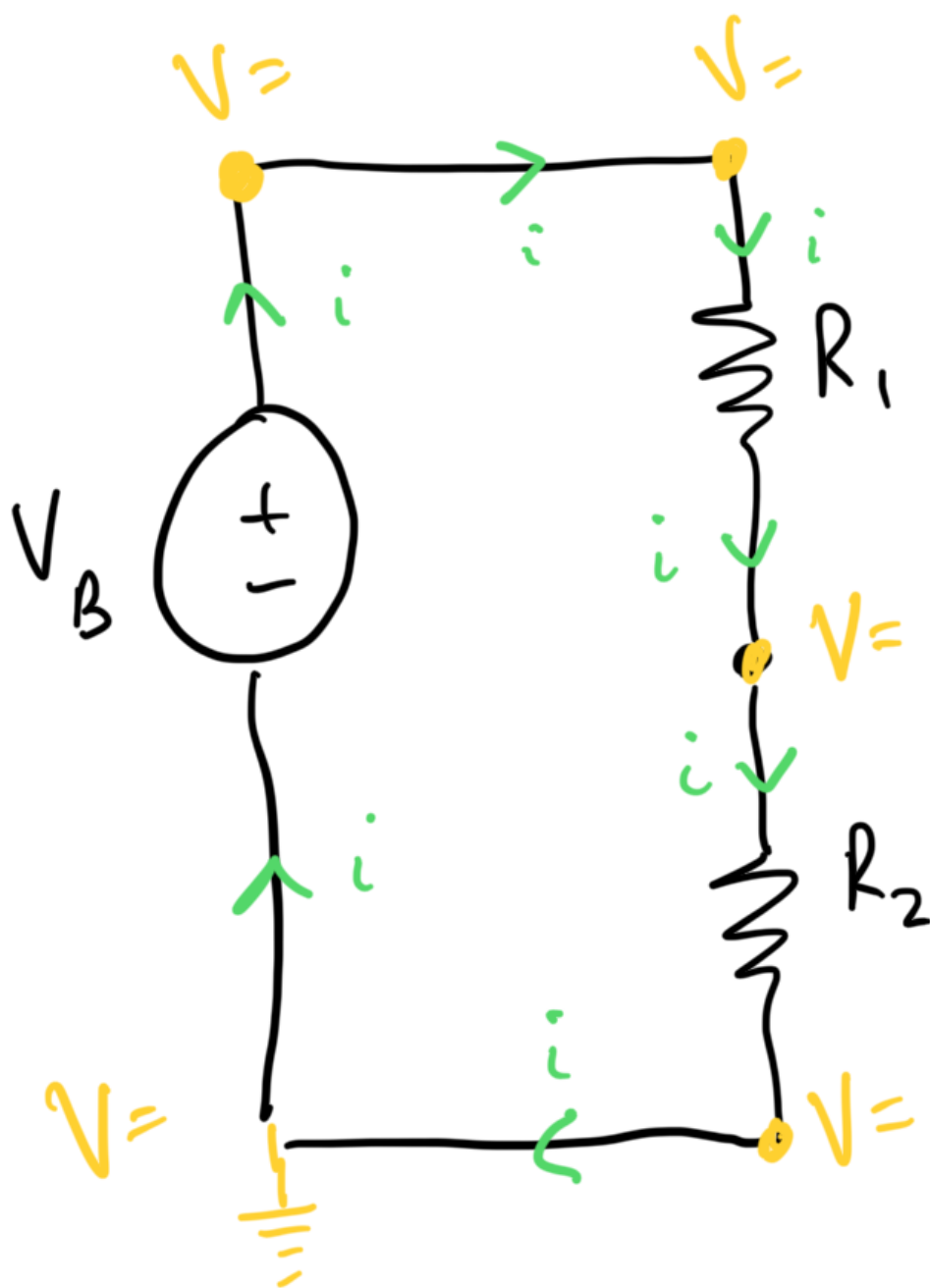


Phys 202 - Resistors in Series and parallel



Imagine connecting
two devices, one
after the other,
in series.

What is i ?

$$\Delta V_{R_1} = i R_1$$

$$V_B - V_m = i R_1$$

$$\underline{\underline{V_m = V_B - i R_1}}$$

$$\Delta V_{R_2} = i R_2$$


$$V_m - 0 = i R_2$$

$$V_B - iR_1 = iR_2$$

$$i(R_1 + R_2) = V_B$$

$$i = \frac{V_B}{R_1 + R_2}$$

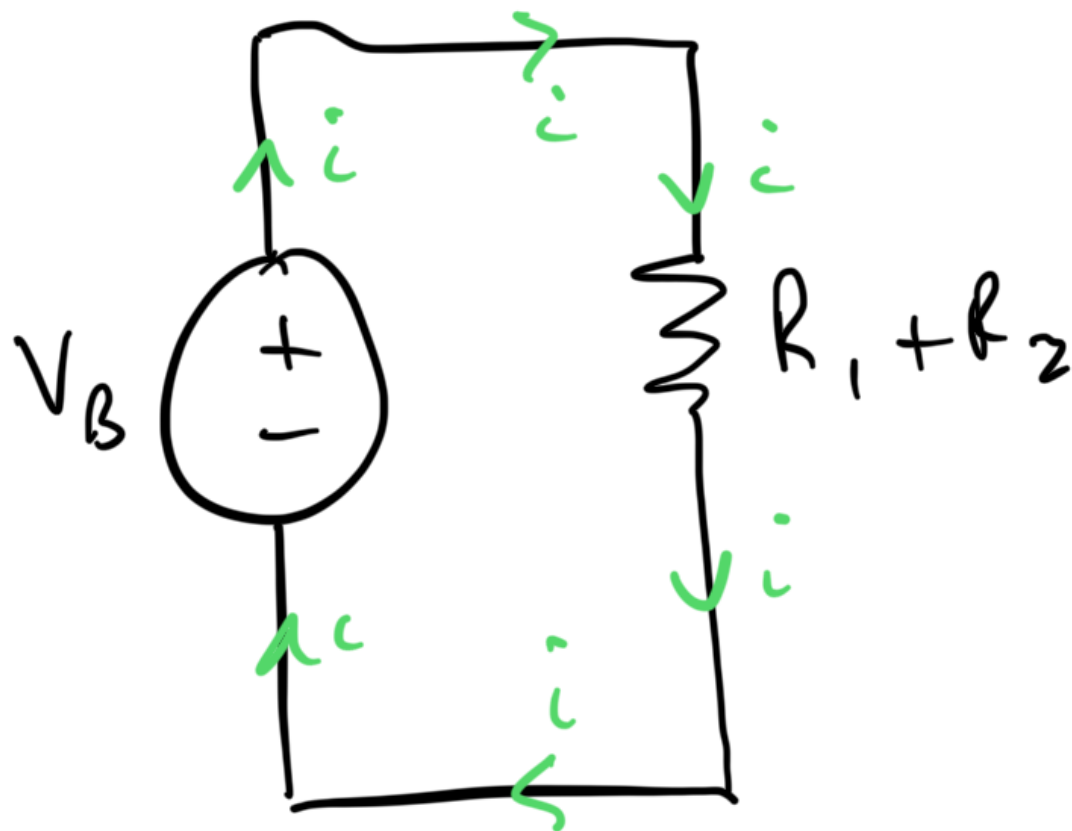
Now, notice that this is equivalent to the following:



Resistors in Series :

$$R_{\text{equivalent}} = R_1 + R_2 + \dots$$

Consider the following circuit:

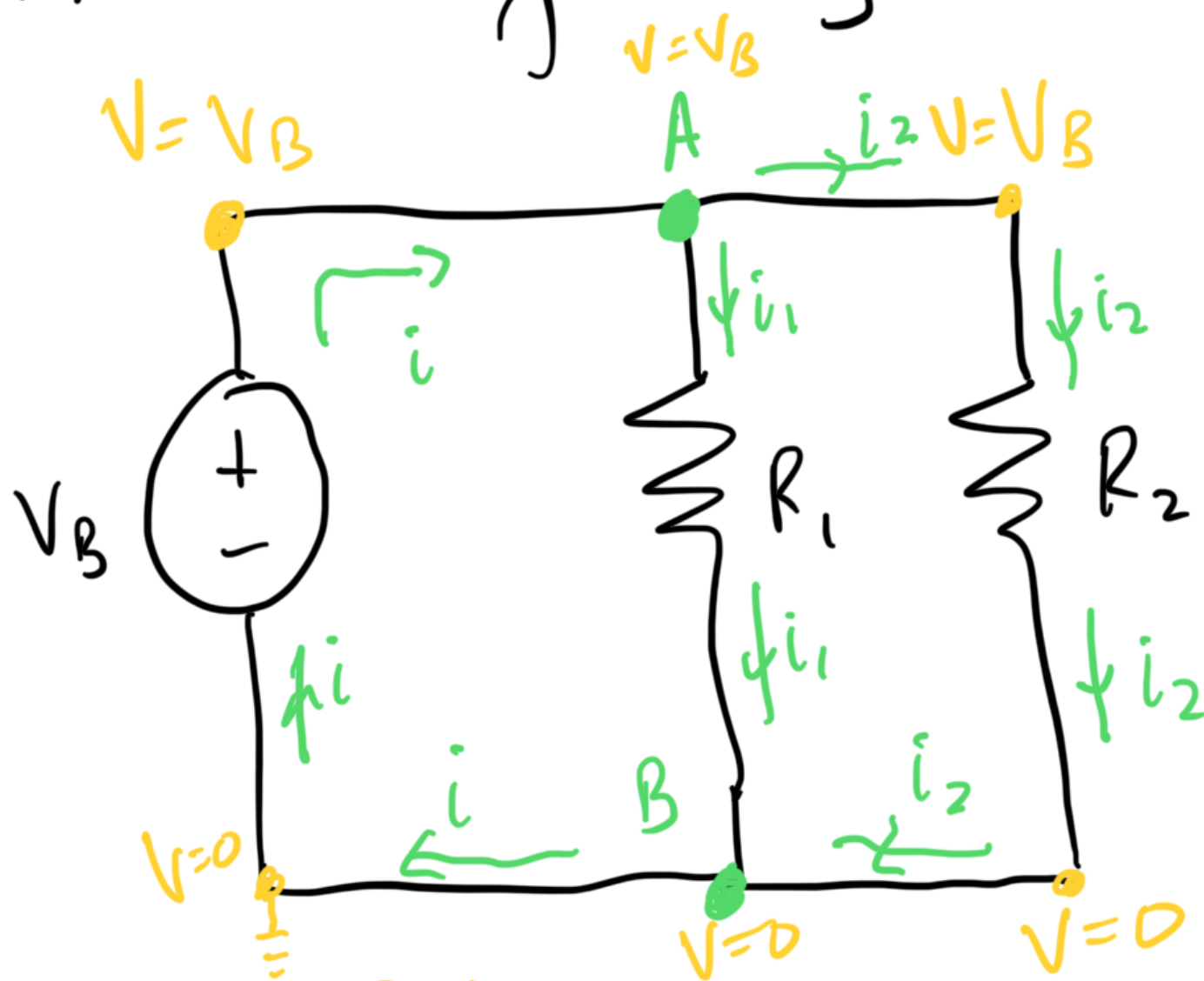

Junction Rule:

Current in = current out

$$\begin{array}{lcl} A: & i = i_1 + i_2 & \\ B: & i_1 + i_2 = i & \end{array} \left. \vphantom{\begin{array}{l} A: \\ B: \end{array}} \right\} \text{consistent}$$

$$\Delta V_{R_1} = i_1 R_1$$

$$V_B - 0 = i_1 R_1 \rightarrow i_1 = \underline{\underline{\frac{V_B}{R_1}}}$$

$$\Delta V_{R_2} = i_2 R_2$$


$$V_B - 0 = i_2 R_2 \rightarrow i_2 = \frac{V_B}{R_2}$$

$$i = i_1 + i_2 = \frac{V_B}{R_1} + \frac{V_B}{R_2}$$

$$i = V_B \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$V_B = i \left(\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \right)$$


Now, this is the same as:

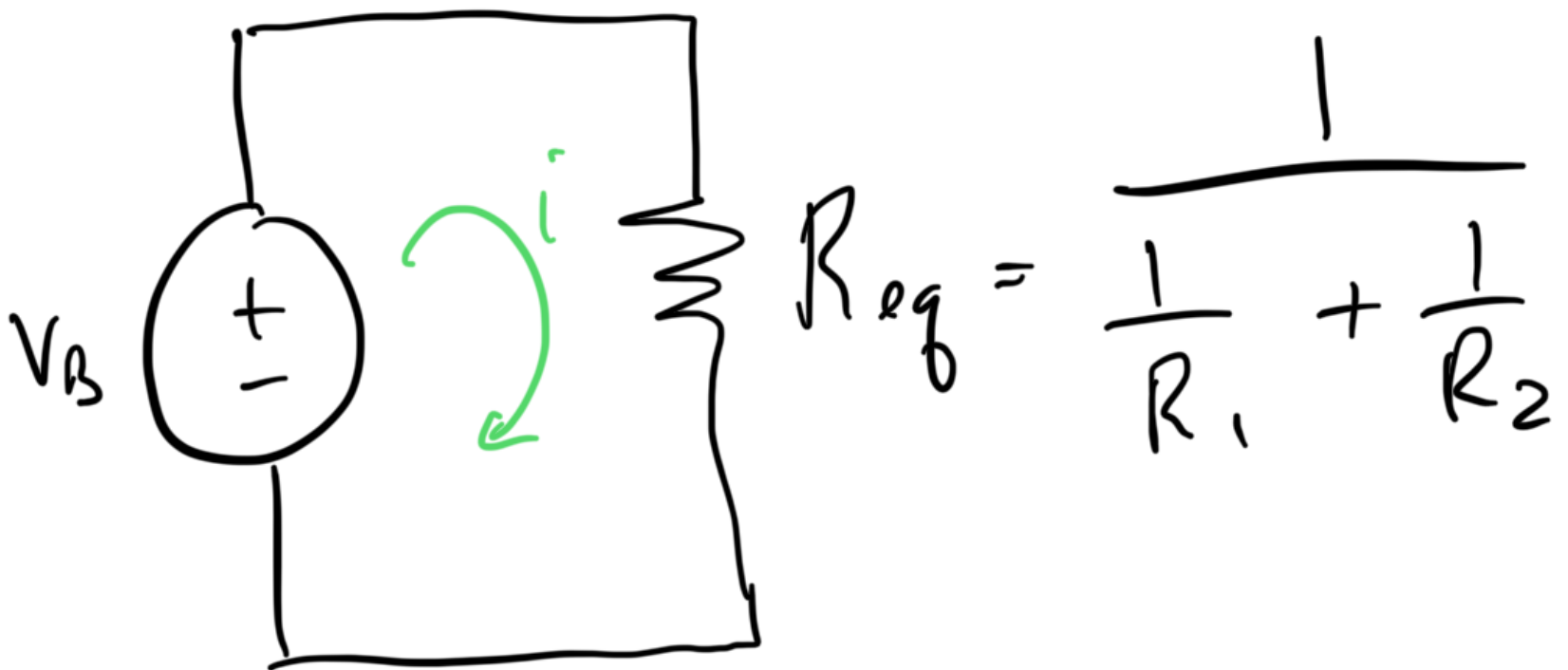

Resistors in Parallel:


$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots}$$

Example:

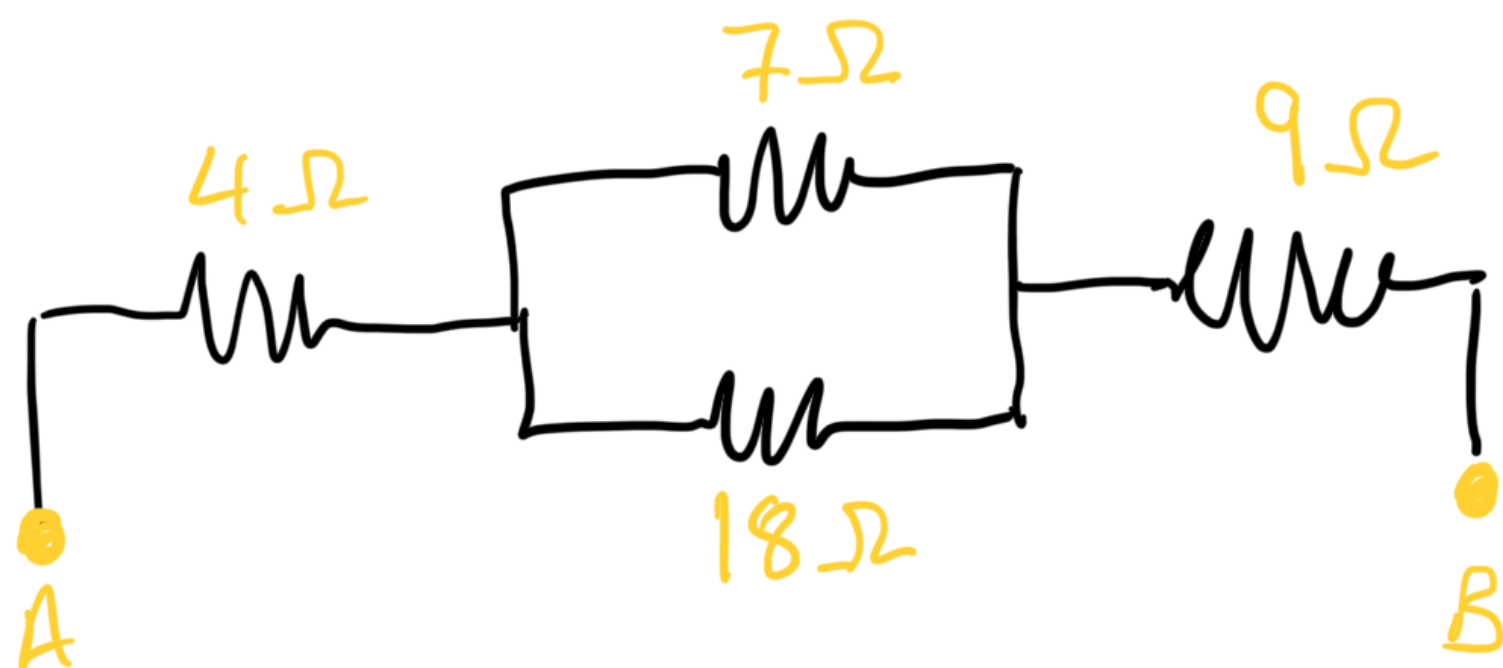

What is the equivalent resistance of this combination?

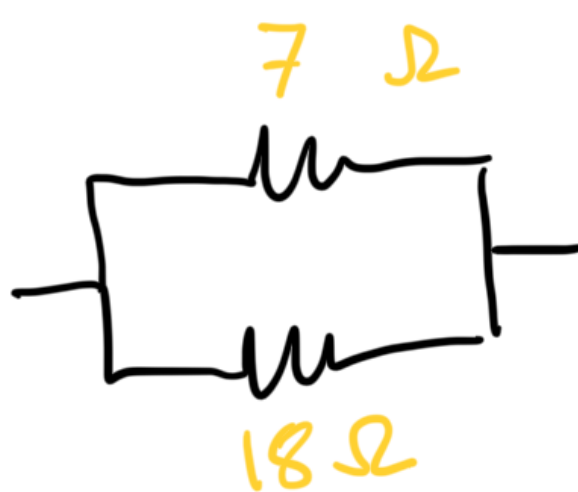- ① Start with the resistors in parallel in the middle.




$$R_{eq} = \frac{1}{\frac{1}{7} + \frac{1}{18}} = 5.04 \Omega$$

- ② Redraw the circuit...



③ Add in Series
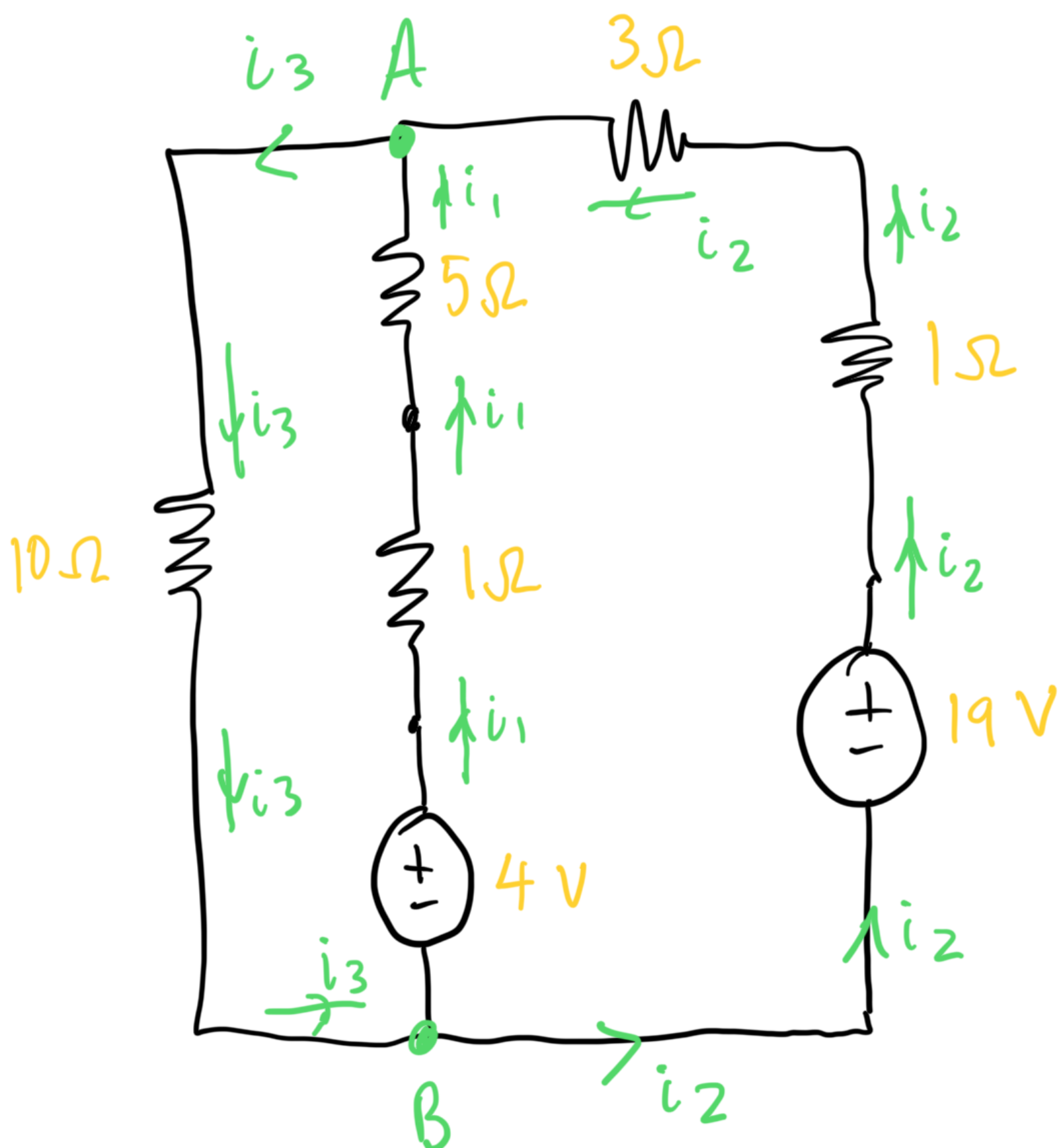
$$R_{eq} = 4\Omega + 5.04\Omega + 9\Omega \\ = 18.04\Omega$$



And also this...

Step 1: Assign currents.


Step 2: Use Junction Rule

$$\begin{array}{l} A: \quad i_1 + i_2 = i_3 \\ B: \quad i_3 = i_1 + i_2 \end{array} \quad \left. \vphantom{\begin{array}{l} A: \\ B: \end{array}} \right\} \text{consistent!}$$

Step 3: Use Loop Rule

— What's the Loop Rule ???

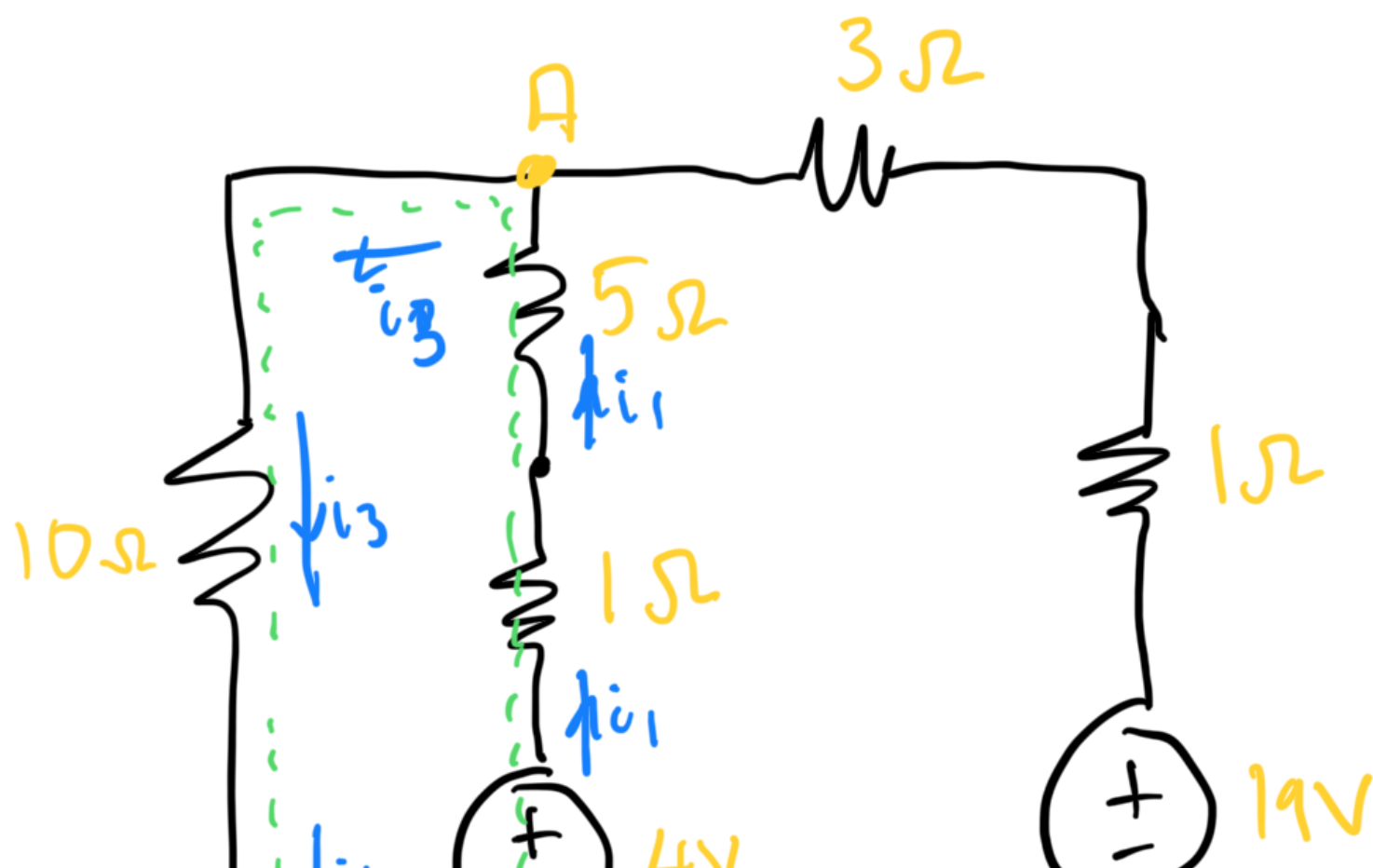"The sum of voltage drops and rises around any closed loop in a circuit is zero."






Start at B, go towards A:

$$+4 - i_1(1) - i_1(5) - i_3(10) = 0$$

Equation 1 $4 - 6i_1 - 10i_3 = 0$

$$-6x + 0y - 10z = -4$$

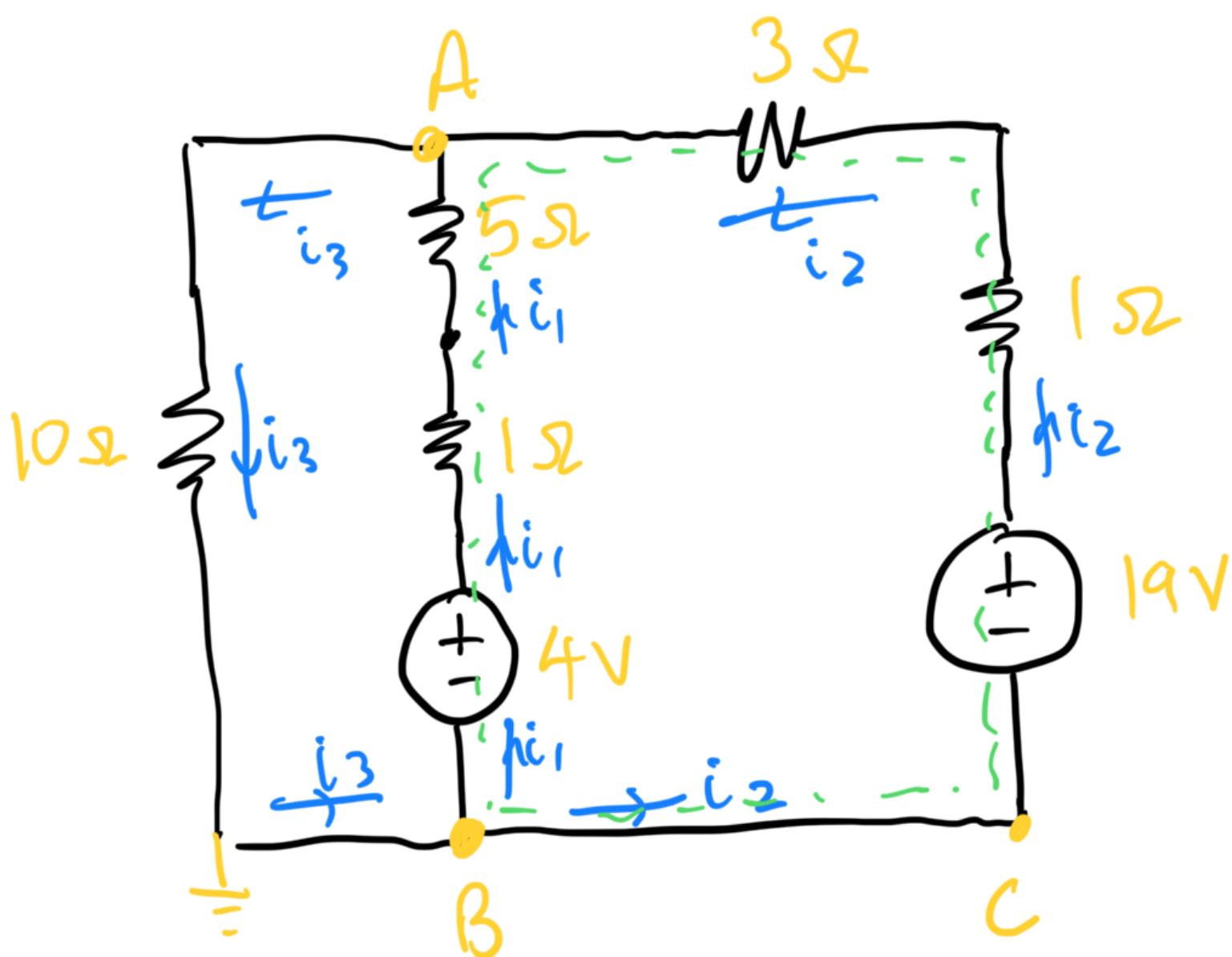

Start at C, go towards A:

$$+19 - i_2(1) - i_2(3)$$

$$+ i_1(5) + i_1(1) - 4$$

$$= 0$$

Equation 2

$$15 - 4i_2 + 6i_1 = 0$$

$$+ 6x - 4y + 0z = -15$$

Equation 3

$$i_1 + i_2 - i_3 = 0$$

$$x + y - z = 0$$

3 equations in 3 unknowns !!

Solve for i_1, i_2, i_3

Solution: $i_1 = -1.08 \text{ A}$

$$i_2 = +2.13 \text{ A}$$

$$i_3 = +1.05 \text{ A}$$

What does this tell us...

Well, apparently we got the direction of i_1 wrong 😊


But that's cool, because math saved us ... YAY!!!

Example Websites:


[system equation calculator - Wolfram|Alpha](#)

[3 Unknown Calculator](#)

Let's go back to Question 7:

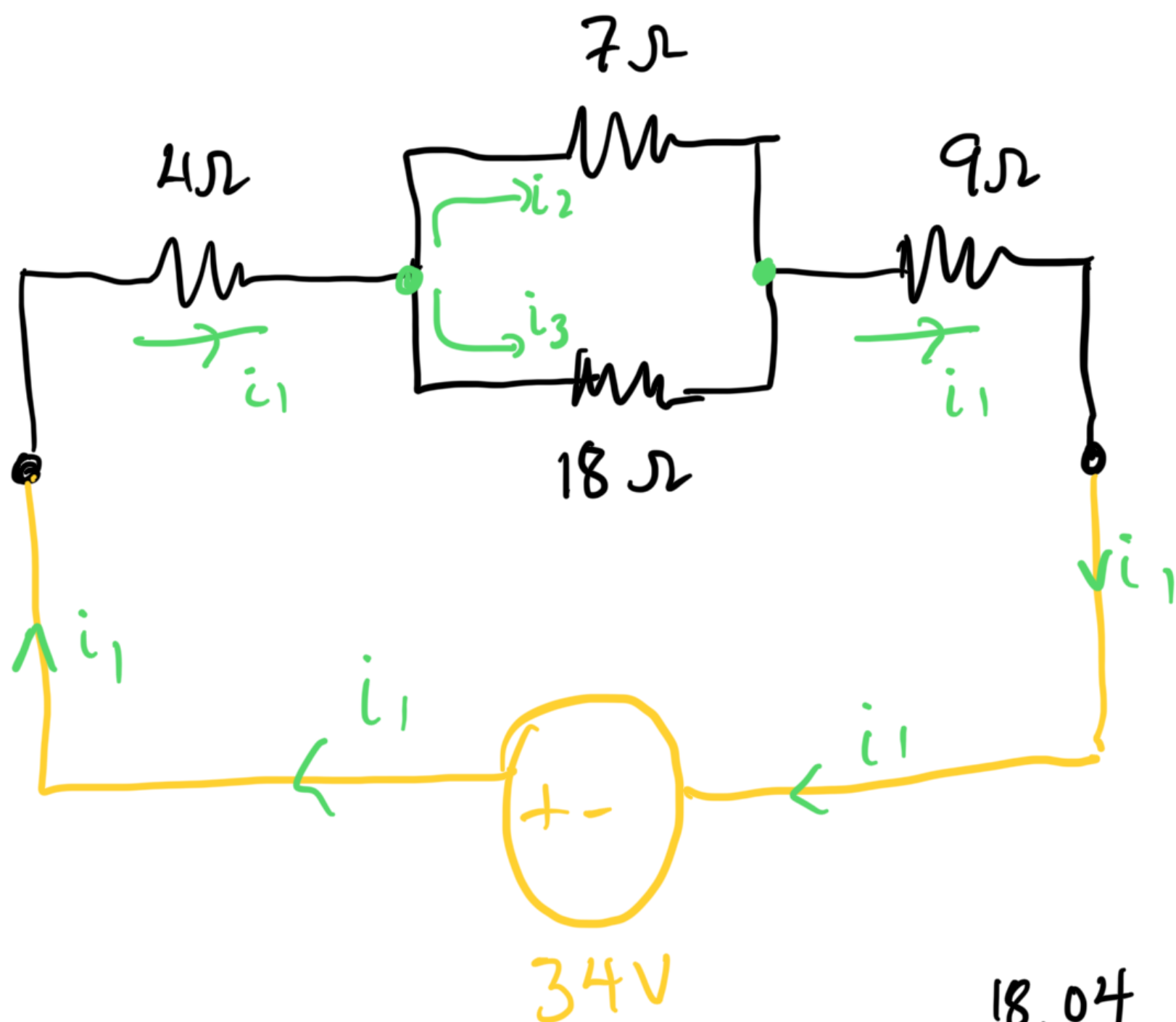



a) $R_{eq} = 18.04 \Omega$

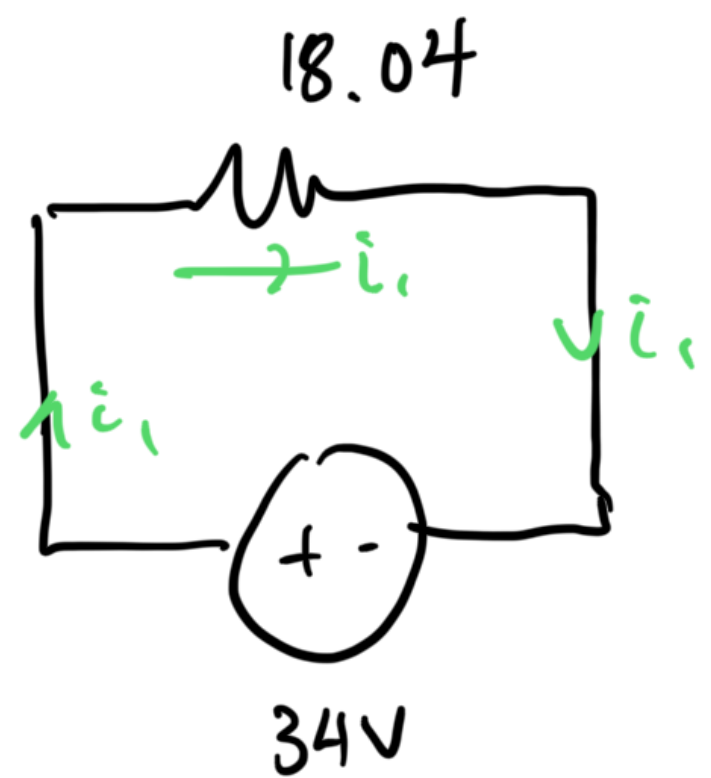

$$i_1 = \frac{34 \text{ V}}{18.04 \Omega} = 1.8847 \text{ A}$$

b)

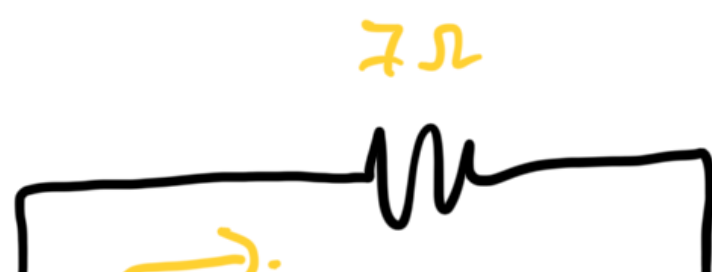

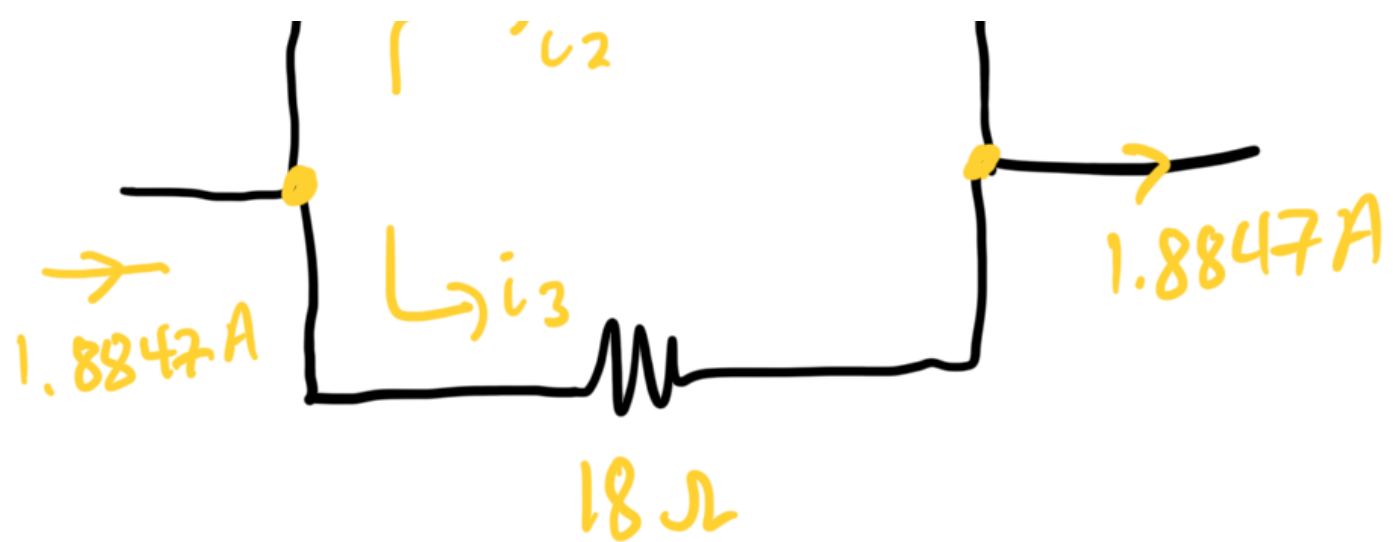

$$\Delta V_7 = 7i_2 = \Delta V_{18} = 18i_3$$

$$\therefore 7i_2 = 18i_3 \quad \therefore i_3 = \frac{7}{18} i_2$$

$$i_2 + i_3 = 1.8847$$

$$i_2 + \frac{7}{18} i_2 = 1.8847$$

$$i_2 = 1.3570\text{ A}$$

$$i_3 = 0.5277\text{ A}$$