## Even More Ciruits

 $\frac{7}{1000}$ AR  $\frac{7}{1000}$ AR  $\frac{7}{1000}$ AR  $\frac{1}{1000}$ BR  $\frac{1}{7}$  = 17.1200

$$i = \frac{34V}{17.122} = 1.986 \text{ A}$$
 $17.122$ 
 $72$ 
 $40$ 
 $40$ 

Whot re i, i, i, ??

$$\Delta V_{co} = i_1(7) = i_2(10)$$

$$i_1 = \frac{10}{7}i_2$$

$$Also, i = i_1 + i_2$$

$$= \frac{10}{7}i_2 + i_2$$

Transform: i, -> x i2-> y 13-> 2 iq->t

3 
$$-bx - 10y = -25$$

$$i_{1} = 1.42 A$$
 $i_{2} = 0.58 A$ 
 $i_{3} = 1.16 A$ 

E Current Hurugh
26 DZ

incata.

b)  $\Delta V_A = 10i_2 = 5.8 V$ 

Wait... We can't solve this are so easily with Falstad. com! This is a DESIGN problem!

 $i^{2}$ 

6 - iR3 - iR2 - iR, =  $6 - i(R_2 + R_1 + R_1) = 0$ R3+R2+R1 = 6/i = 6/,001  $R_3 + R_2 + R_1 = 6000$ 

$$\Delta V_{AB} = i_2 R_2 = i_1 R_2$$
  
 $\vdots i_1 = i_2 = i_2/2$ 

$$6 - i R_3 - \frac{i}{2} R_2 - i R_1 = 0$$

$$6 - i (R_3 + \frac{R_2}{2} + R_1) = 0$$

$$R_3 + \frac{R_1}{2} + R_1 = 6/i = \frac{6}{100115}$$

$$-5217.46$$

$$R_3 + R_2 + R_1 = 5217.4$$

$$6 - i R_2 - i R_1 = 0$$

$$R_2 + R_1 = 6/i = \frac{6}{.0019}$$

$$= 3157.89$$

$$R_{2} + R_{1} = 3157.89$$

$$R_{3} + R_{2} + R_{1} = 6000.00$$

$$R_{3} + \frac{R_{2}}{2} + R_{1} = 5217.40$$
2

$$\frac{(1-2)}{2} = \frac{6000 - 5217.40}{2}$$

$$R_2 = 1565.2 \text{ L}$$

$$= 1.565 \text{ kg}$$

$$R_1 = 1592.672$$

$$= 1.592 22$$

## Interesting desour votion:

So, sometimes, it we use current in mA and resistance in kSL

it will work out untely!!
We could have done that in this
problem, in fact.